

# **ELECENG 2CF3: Assignment 1**

Name: Gurleen Kaur Rahi


Student ID: 400377038

MacId: rahig

## Exercise #1: Inverting Op-amp circuit

### Section 1. A:
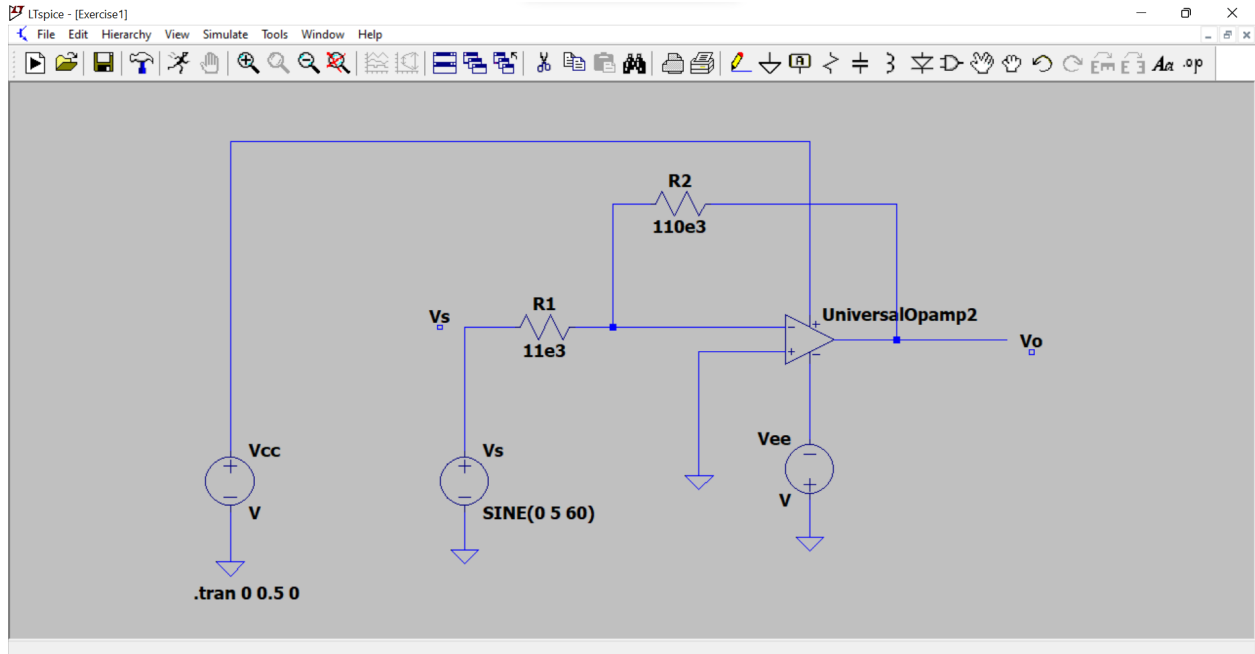
#### 1. Include an image of your schematic.




#### 2. Copy and Paste the complete netlist into your report. This serves as a textual summary of your circuit and thus helps with assigning part marks to incorrect submissions.

```
Vs N004 0 SINE(0 5 60)
XUniversalOpamp2 0 N002 N001 N005 N003 level2 Avol=1Meg GBW=10Meg Slew=10Meg
Ilimit=25m Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
R1 N002 N004 11e3
R2 N003 N002 110e3
Vee 0 N005 V
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

## Section 1. B

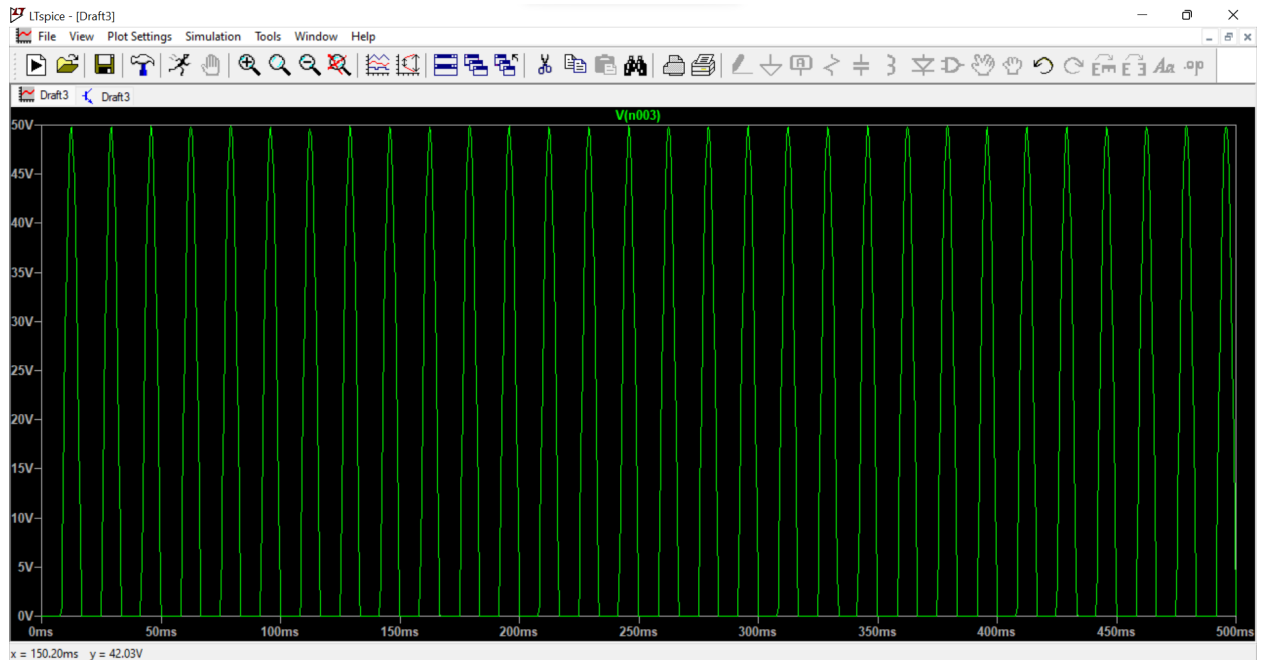1. Include the plot for  $V_o$  as a function of time.



2. Copy and Paste the complete netlist into your report.


```
Vcc N001 0 100
Vs N004 0 SINE(0 5 60)
XU1 0 N002 N001 N005 N003 level2 Avol=1Meg GBW=10Meg Slew=10Meg Ilimit=25m
Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
R1 N002 N004 11e3
R2 N003 N002 110e3
Vee 0 N005 0
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

3. Explain the behavior of  $V_o$ . State which half-periods of  $V_s$  (the positive or the negative) are amplified and transferred to the output and which are clipped.

$V_o$  receives a sinusoid input, but because  $V_{cc}$  is 100 V and  $V_{ee}$ , the negative voltage, is zero,  $V_o$  does not receive a negative value. Only positive values and zero are available for  $V_o$ , except when a rectifier is involved and a negative value is intended. The positive values are trimmed for the graph above, while the negative values of the  $V_s$  scale are exaggerated.

## Section 1. C
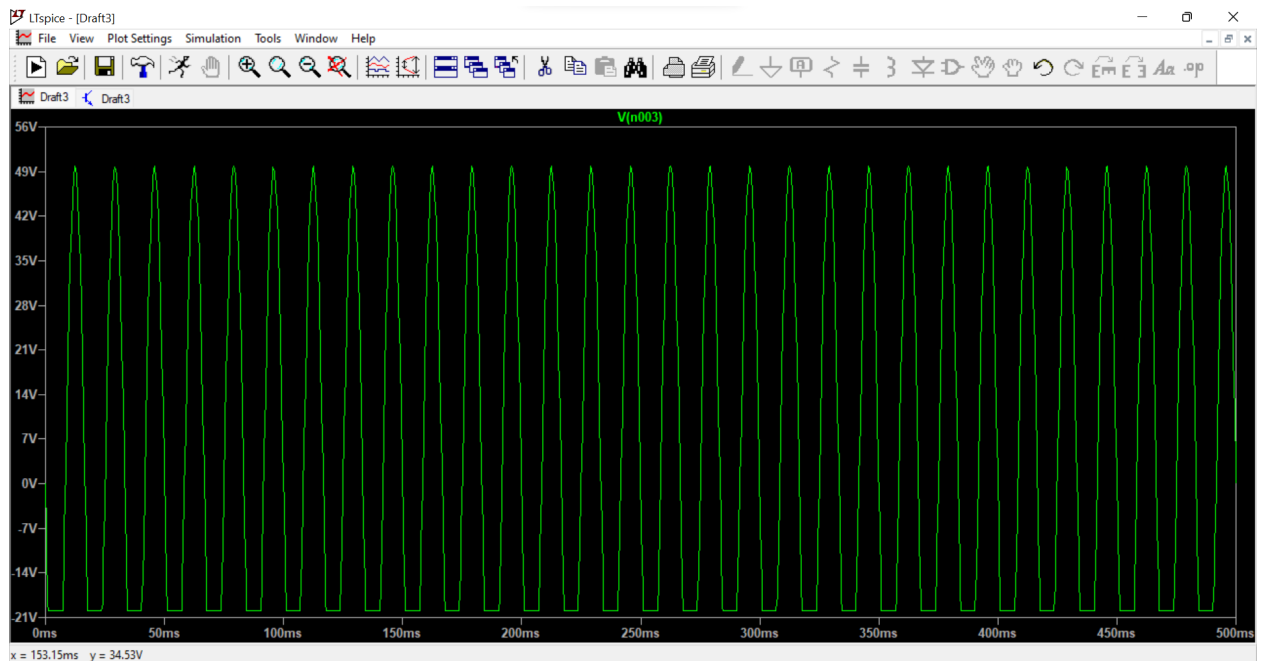
### 1. Include the plot for $V_o$ as a function of time.



### 2. Copy and Paste the complete netlist into your report.


```
Vcc N001 0 100
Vs N004 0 SINE(0 5 60)
XU1 0 N002 N001 N005 N003 level2 Avol=1Meg GBW=10Meg Slew=10Meg Ilimit=25m
Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
R1 N002 N004 11e3
R2 N003 N002 110e3
Vee 0 N005 20
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

3. Explain the behavior of  $V_o$ . State which half-periods of  $V_s$  (the positive or the negative) are amplified and transferred to the output and which are clipped.

From the graph of  $V_o$ , it is seen that  $V_o$  has a sinusoidal behavior. The graph is clipped at -20 V and the values between +5 and -2 are amplified which is further transferred to the output of the circuit. The values that are clipped from the graph are -2 and -5.

## Section 1. D

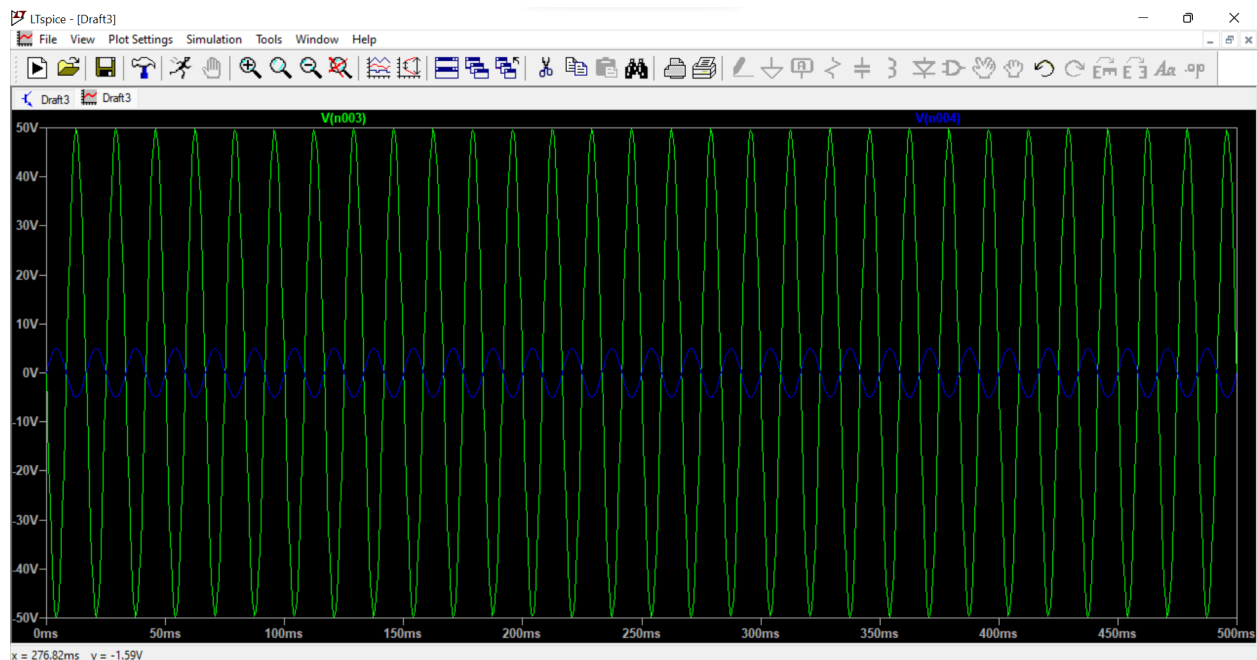1. Include the plot for both  $V_s$  and  $V_o$  as functions of time. Put both waveforms on the same plot.




2. Copy and Paste the complete netlist into your report.

```
Vcc N001 0 100
Vs N004 0 SINE(0 5 60)
XU1 0 N002 N001 N005 N003 level2 Avol=1Meg GBW=10Meg Slew=10Meg Ilimit=25m
Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
R1 N002 N004 11e3
R2 N003 N002 110e3
Vee 0 N005 100
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
```


.end

## Section 1. E

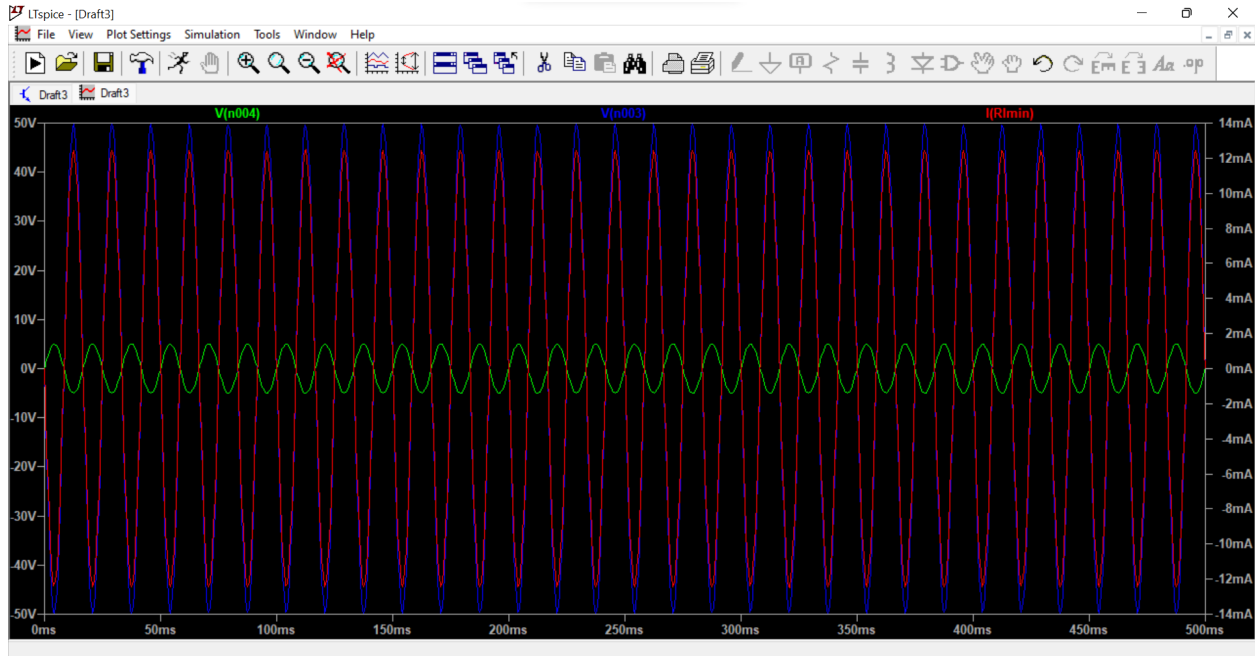1. For the case of  $R_L = 2R_{L, \min}$ , include the plot of  $V_s$ ,  $V_o$ , and  $I_o$  as functions of time.  
Put all three waveforms in one plot.



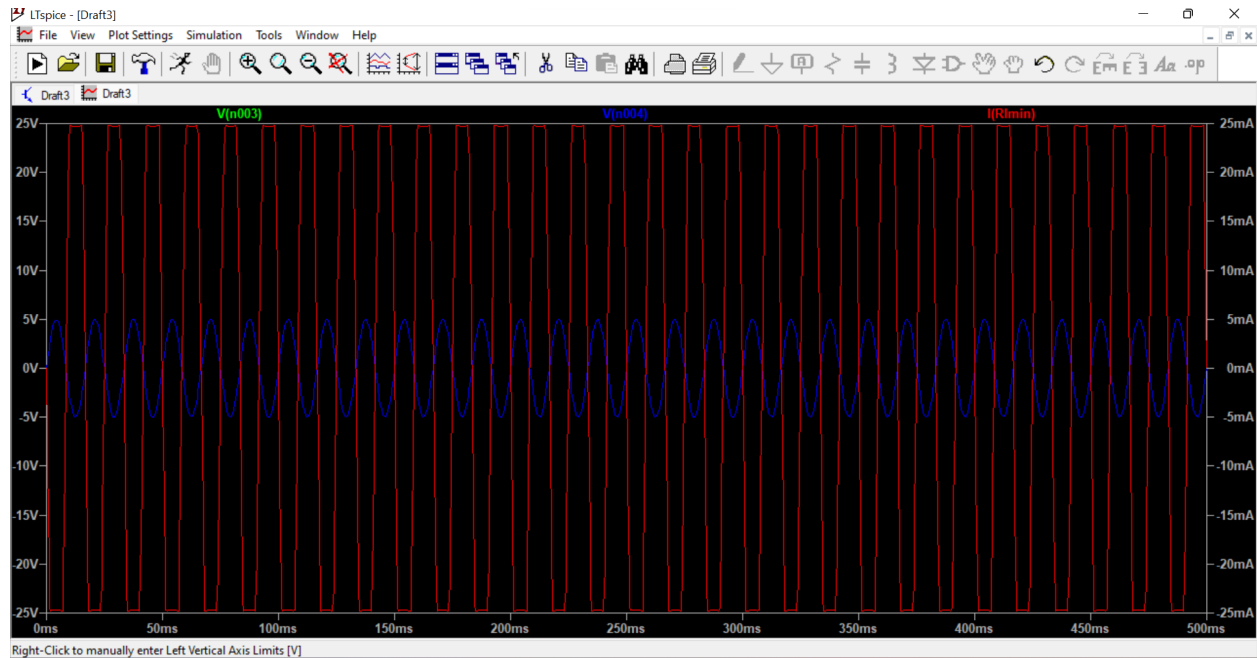2. For the case of  $R_L = 0.5R_{L, \min}$ , include the plot of  $V_s$ ,  $V_o$ , and  $I_o$  as functions of time.  
Put all three waveforms in one plot.



### 3. Copy and paste the complete netlist into your report.

```
Vcc N001 0 100
Vs N004 0 SINE(0 5 60)
XUniversalOpamp2 0 N002 N001 N005 N003 level2 Avol=1Meg GBW=10Meg Slew=10Meg
Ilimit=25m Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
R1 N002 N004 11e3
R2 N003 N002 110e3
Vee 0 N005 100
RLmin N003 0 1e3
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

### 4. Show the derivation of $R_{L, \min}$ .

$$\text{Max } V = 50V$$

$$\text{Current} = 25mA$$

$$R_{L\min} = \frac{50V}{25mA} = 2k\Omega$$

**5. State the observed maximum value of  $V_o$  in the case of  $R_L = 2R_{L,\min}$ .**

The observed maximum value of  $V_o$  is 50V.

**6. State the observed maximum value of  $V_o$  in the case of  $R_L = 0.5R_{L,\min}$ .**

The observed maximum value of  $V_o$  is 25V.

**7. Comment on whether there is a difference between your observations in parts 5 and 6.**

Yes, there is a difference between my observations in both parts.

**8. Explain why you observe this difference (if any) referring also to the observed maximum values of  $I_o$  in both cases.**


Because since  $R_L$  was  $2R_{L\min}$ , the current was equal to 12.5mA approximately. However when it changed to  $0.5R_{L\min}$ , the current increased by 2 times and it was 13mA. This relates to Ohm's law since the voltage was held constant.

## **Exercise #2: Non-Inverting Op-amp circuit**

### **Section 2. A**

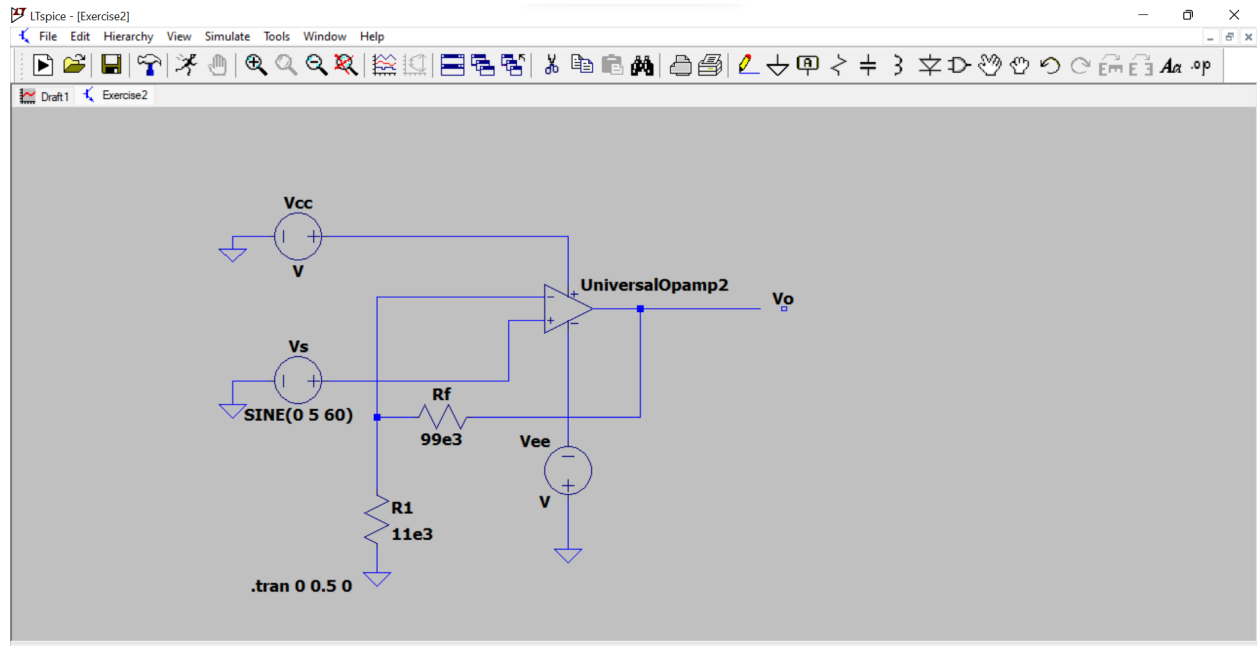**1. Include an image of your schematic.**






## 2. Provide the complete netlist.

```
Vcc N001 0 V
XUniversalOpamp2 N004 N002 N001 N005 N003 level2 Avol=100 GBW=10Meg Slew=10Meg
Ilimit=25m Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
Vee 0 N005 V
R1 N002 0 11e3
Rf N003 N002 99e3
Vs N004 0 SINE(0 5 60)
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

## Section 2. B
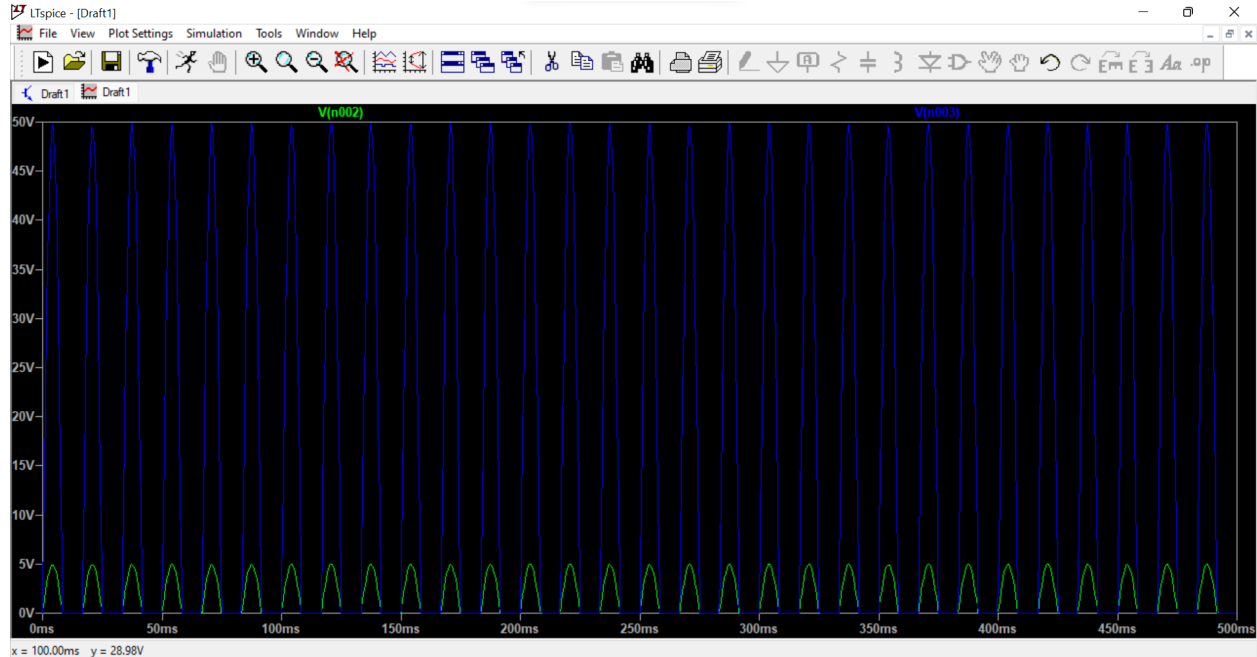
### 1. Include the plot of $V_s$ and $V_o$ . Put both waveforms in one plot.



**2. Provide the complete netlist.**

```
Vcc N001 0 100
Vs N004 0 SINE(0 5 60)
XUniversalOpamp2 N004 N002 N001 N005 N003 level2 Avol=1Meg GBW=10Meg
Slew=10Meg Ilimit=25m Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
Vee 0 N005 0
R1 N002 0 11e3
Rf N003 N002 99e3
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

**3. State whether your circuit achieved the required gain of 10.**


Yes, the circuit has achieved the required gain of 10 since the max value of  $V_s$  is 50V and that of  $V_o$  is 5 V. Therefore,  $V_s$  is 10 times that of  $V_o$ .

**4. State whether it is operating in a nonlinear regime. Justify your statement.**

It is not operating in a nonlinear regime because the voltage of output to input is constant which is the required gain of 10.

## Section 2. C
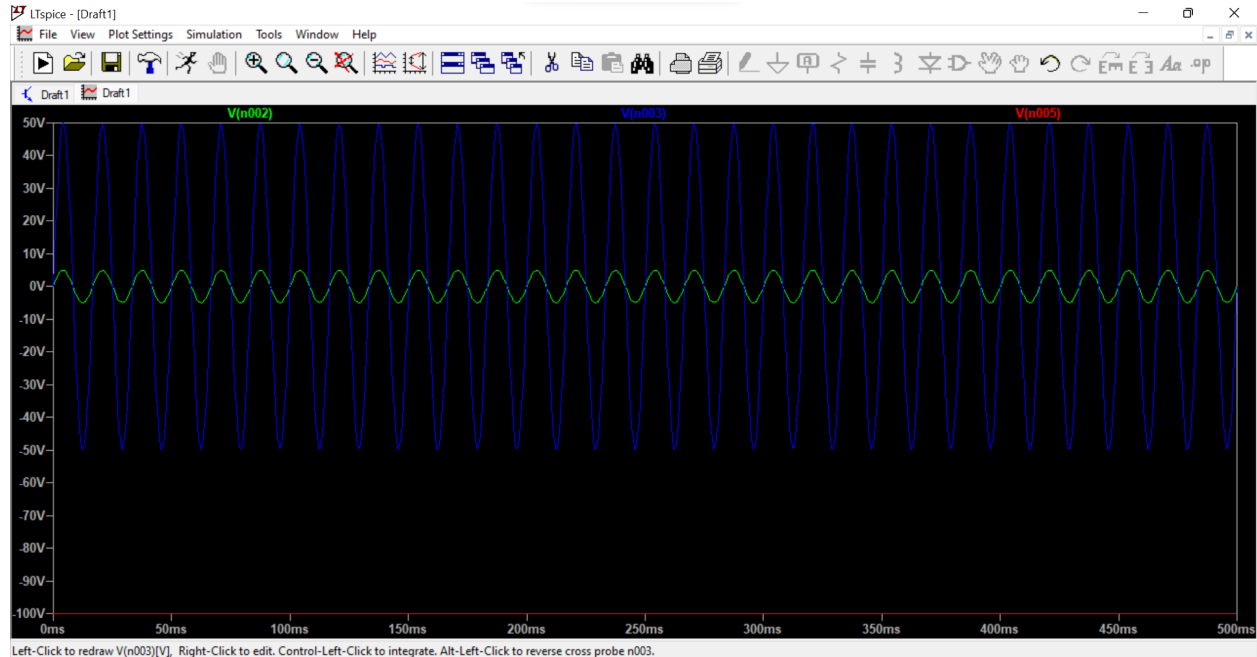
### 1. Include the plot of $V_s$ and $V_o$ . Put both waveforms in one plot.



### 2. Provide the complete netlist.

```
Vcc N001 0 100
Vs N004 0 SINE(0 5 60)
XUniversalOpamp2 N004 N002 N001 N005 N003 level2 Avol=1Meg GBW=10Meg
Slew=10Meg Ilimit=25m Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
Vee 0 N005 100
R1 N002 0 11e3
Rf N003 N002 99e3
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

### 3. State whether your circuit achieved the desired gain of 10.


Yes, the circuit has achieved the desired gain of 10 as we can see that in the graph  $V_s$  is 5 V and  $V_o$  is approximately equal to 5 V.

**4. State whether it is operating at a nonlinear regime. Justify your statement.**

It is not operating at a nonlinear regime because the voltage of output to input is constant which is equal to 10, the same as the required gain.

**Section 2. D**

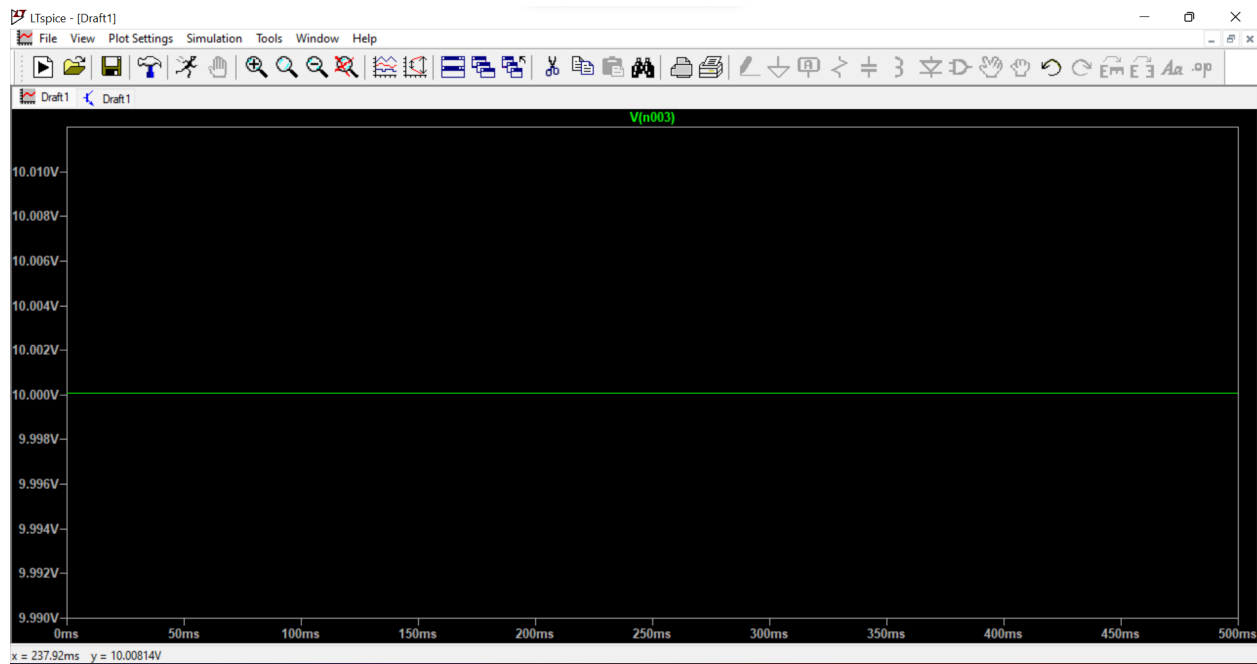
**1. Include the plot for  $V_o$  for the case of  $A_o = 10^6$ .**



**2. Provide the complete netlist for the case of  $A_o = 10^6$ .**

```
Vcc N001 0 100
XUniversalOpamp2 N004 N002 N001 N005 N003 level2 Avol=1meg GBW=10Meg
Slew=10Meg Ilimit=25m Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
Vee 0 N005 100
R1 N002 0 11e3
Rf N003 N002 99e3
Vs N004 0 1
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

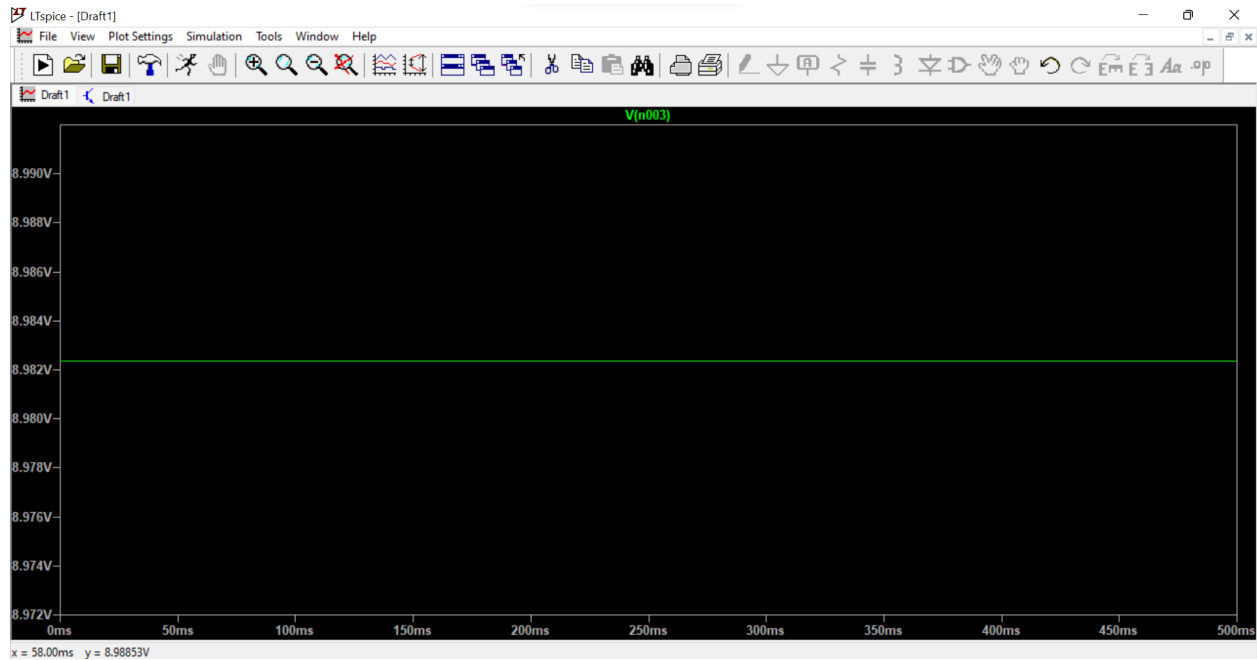**3. Include the plot for  $V_o$  for the case of  $A_o = 100$ .**



**4. Provide the complete netlist for the case of  $A_o = 100$ .**

```
Vcc N001 0 100
XUniversalOpamp2 N004 N002 N001 N005 N003 level2 Avol=100 GBW=10Meg Slew=10Meg
Ilimit=25m Rail=0 Vos=0 En=0 Enk=0 In=0 Ink=0 Rin=500Meg
Vee 0 N005 100
R1 N002 0 11e3
Rf N003 N002 99e3
Vs N004 0 1
.tran 0 0.5 0
.lib UniversalOpAmp2.lib
.backanno
.end
```

**5. State the simulated circuit gain in the case when  $A_o = 100$ .**

The simulated circuit gain in the case when  $A_o = 100$  is approximately 8.983.

**6. State the gain error percentage compared to the ideal gain of 10.**

$$\begin{aligned} \text{Gain error percentage} &= ((\text{Actual gain} - \text{ideal gain}) / \text{ideal gain}) * 100\% \\ &= ((8.983 - 10) / 10) * 100 = \mathbf{10.17\%} \end{aligned}$$

